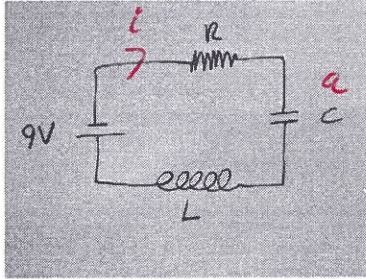


Name

- Write down ODE for the circuit.



$$i = q'$$
$$V_R = iR \quad V_C = q/C \quad V_L = L i'$$

~~Write down ODE for the circuit.~~

$$9 + Rq' + \frac{q}{C} + Lq'' = 0$$

1. Write down and solve the ODE for the circuit with the inductor replaced by a wire.

■ Solve $y' = 2y + e^t$ $y(0) = 1$

2. Solve $y' + 2ty = te^{-t^2}$